

The background is a blue-toned image of a circuit board. A central black rectangle with rounded corners contains the title and author information in white text. The circuit board features various traces, pads, and components, with some elements highlighted in a lighter blue color.


# OPEN COLLECTOR CIRCUIT

JUSTICE MCNEELEY

RBT 125
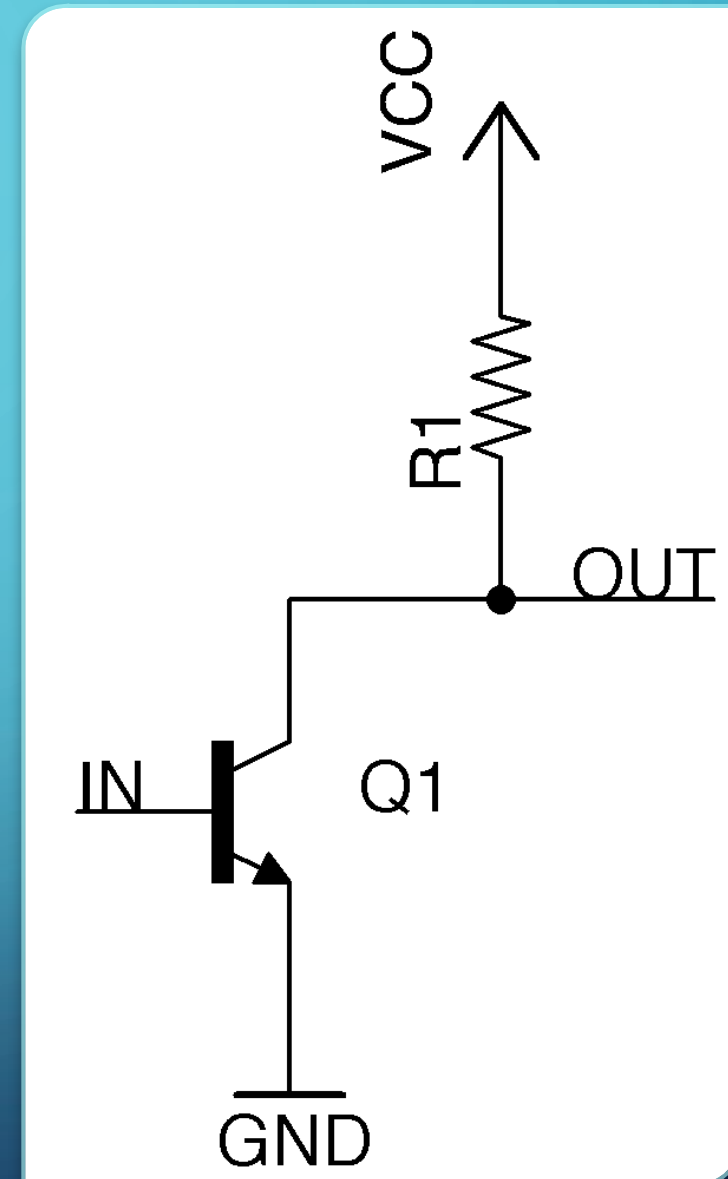
# INTRODUCTION TO OPEN COLLECTOR CIRCUIT


- Enables efficient and dependable inter-component communication.
- Composed of a transistor and a resistor.
- Together, they form an open circuit that responds to an external signal.
- Can act as either a switch or amplifier based on its setup.
- Found in numerous applications, from basic digital logic gates to complex power supply systems.
- An in-depth grasp of these circuits paves the way for designing more effective and reliable electronic infrastructures.


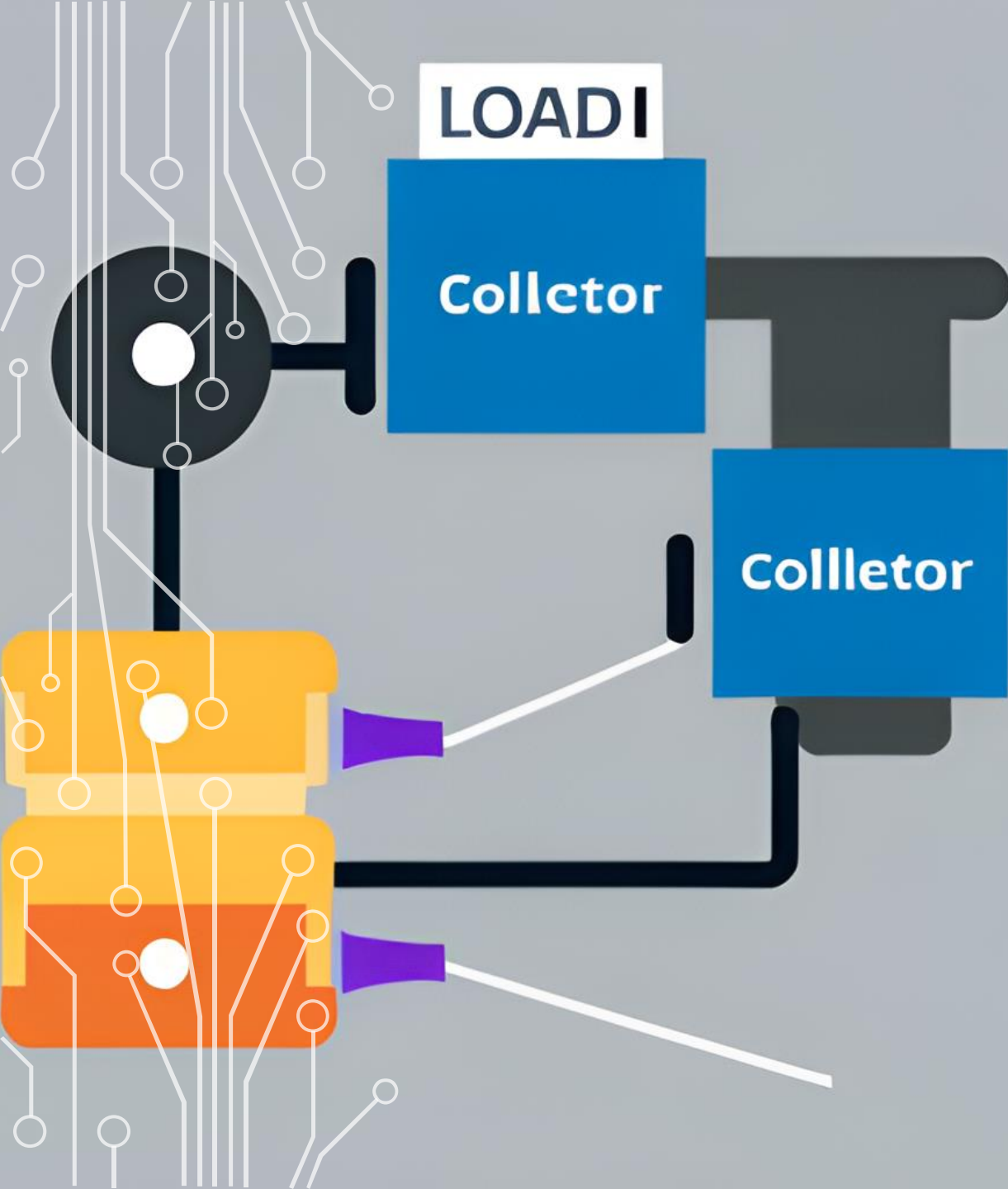
# FUNCTION OF OPEN COLLECTOR CIRCUIT

- Controls the flow of current within an electronic device.
- Contains a transistor, acting as a switch, and a resistor to limit current flow.
- When the transistor is on: Current flows from the power source, through the resistor, to the controlled device.
- When the transistor is off: No current passes through the circuit.
- Widely used in precision-required devices like sensors and instrumentation.
- Essential in high-speed operations such as computers and digital devices.
- Offers enhanced flexibility in current control.
- Provides protection against potential device overloading.






# WHERE OPEN COLLECTOR CIRCUIT IS USED

## 1. Digital Electronics Interface:

- Bridging the gap between different voltage levels.
- Example: Connecting a 5V microcontroller to a 3.3V device safely.

## 2. Driving LEDs and Low-Power Devices:

- Connects the open collector output to an LED's cathode using a current-limiting resistor.
- Enables LED control based on the logic level of the open collector output.
- Frequently employed in indicator lights and basic displays.



## ADVANTAGES OF OPEN COLLECTOR CIRCUIT

### Handling Higher Voltage Levels:

- Capable of managing voltages that exceed the limits of many other circuit types.
- Perfect for high-voltage applications such as power supplies and motor controls.

### Simplicity and Cost-Effectiveness:

- Fewer components compared to other circuit types.
- Leads to a decrease in overall circuit cost.
- Simplifies the design and manufacturing process.



# DISADVANTAGES OF THE CIRCUIT

## 1. Need for External Pull-Up Resistor:

- Essential for proper functioning.
- Introduces added complexity and can increase circuit design cost.

## 2. Limitations on Driving High-Current Loads:

- Cannot directly handle high-current loads.
- Restricts their applicability in certain scenarios or devices.



# VARIATIONS OF THE CIRCUIT

## 1. Darlington Configuration:

- Incorporates multiple transistors.
- Provides enhanced current gain and superior output current potential.
- Ideal for applications like motor driving or high-power LED operation.

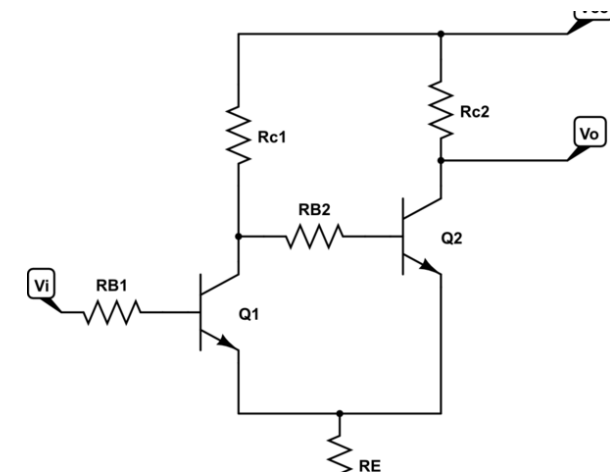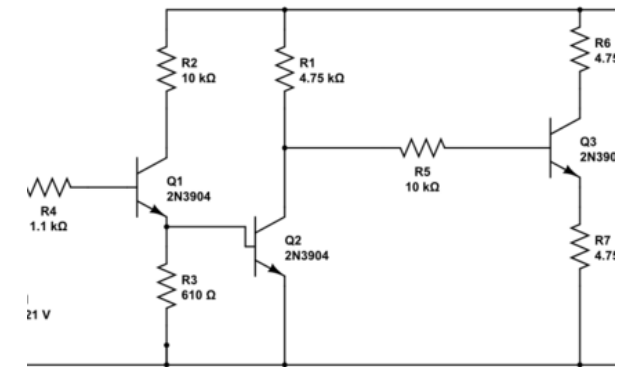
## 2. Schmitt Trigger Integration:

- Introduces hysteresis to the circuit.
- Helps diminish noise and bolsters circuit stability.
- Especially valuable in switch debouncing or signal conditioning tasks.



# PULL-UP RESISTORS

## Pull-up resistor

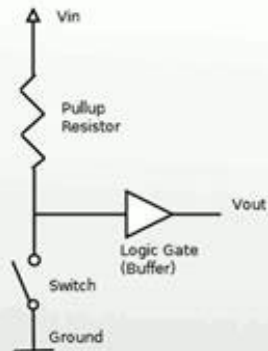


[https://en.wikipedia.org/wiki/File:Pullup\\_Resistor.png](https://en.wikipedia.org/wiki/File:Pullup_Resistor.png)

- Provides a current path when the transistor is turned off.
- Compensates for the open circuit behavior of the transistor in its off state.
- Connection to the Positive Voltage Rail:
- Ensures the circuit's continuity by allowing current to flow even when the transistor is off.
- Dictates the amount of current flowing through the circuit when the transistor is off.
- A value too high can impair the circuit's functionality.
- A value too low risks overcurrent and potential damage to the transistor.
- The correct resistor value is paramount, demanding careful selection based on the specific needs and specifications of the circuit in use.



- Open collector circuits pull the output to a low voltage.
- Push-pull circuits have the capability to both push and pull the output.
- Open collector circuits are often chosen for scenarios where there's already a high voltage level, and only a low voltage needs to be pulled down.
- Resembles push-pull circuits but integrates an extra transistor.
- This extra transistor ensures that not both transistors are active simultaneously, avoiding a short-circuit condition.
- Totem pole circuits generally offer a steadier output in comparison to push-pull circuits.
- Totem pole circuits tend to consume more power.
- Open collector circuits are often the preferred choice for low-power applications needing a straightforward and dependable solution.

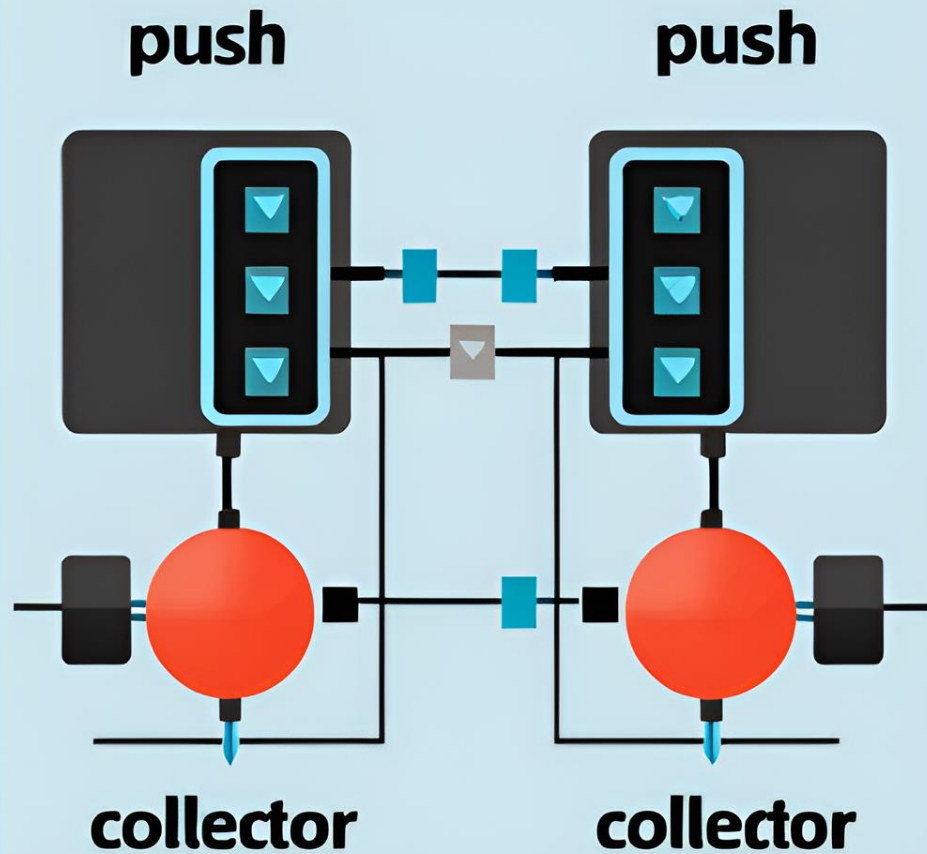



# EXAMPLES OF OPEN COLLECTOR CIRCUITS

## 1. Transistor-Transistor Logic (TTL) Digital Circuit:

- Features an open collector setup where the output of one transistor is tied to the input of another.
- Facilitates seamless interfacing among different TTL circuits.
- Ensures compatible voltage levels among interconnected components.
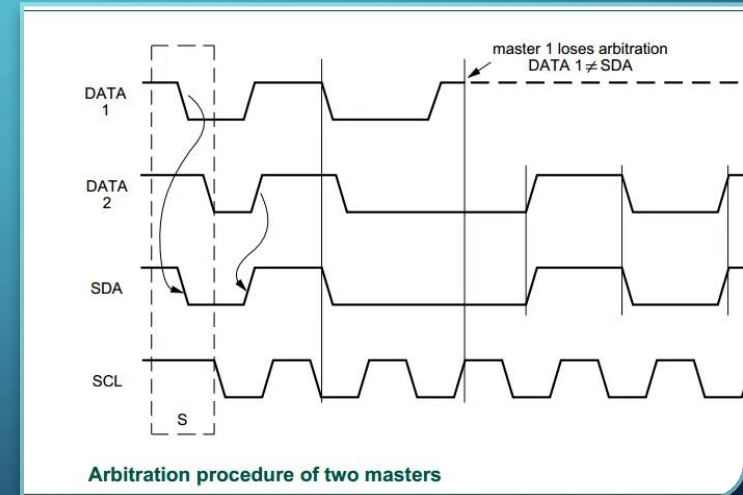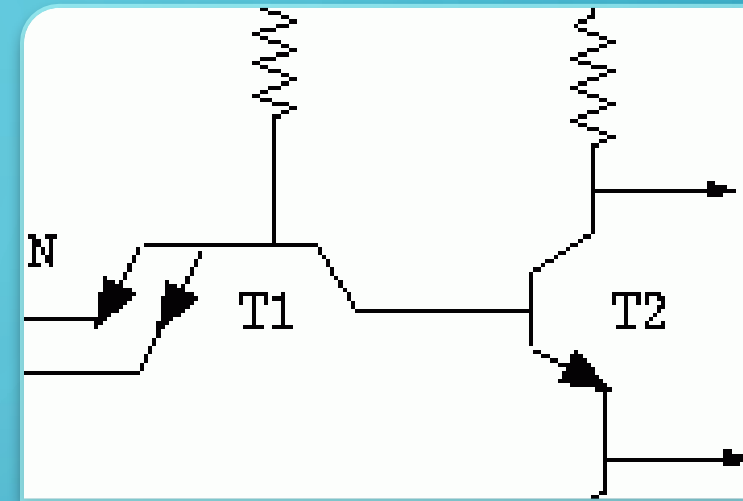
## 2. I2C Bus Communication Protocol:

- Widely used communication standard in numerous electronic devices.
- Leverages open collector outputs, allowing multiple devices to interact on the same bus without mutual interference.
- Optimal for integrating sensors, displays, and other accessories with microcontrollers or digital equipment.





# CONCLUSION

- Open collector circuits play a pivotal role in facilitating efficient communication between diverse electronic devices and components.
- Suited for a wide array of applications, enhancing their relevance in the electronics realm.
- Discussed their operation, the merits and demerits, and various adaptations of these circuits.
- Highlighted the indispensable role of pull-up resistors in these circuits.
- Benchmarked open collector circuits against other prevalent circuit types, emphasizing their unique characteristics.
- Presented tangible examples, like TTL digital circuits and the I2C bus, underscoring their practical utility in everyday electronic devices.

# REFERENCES

- Albert Paul Malvino. (1993). *Electronic Principles*. Simon & Schuster Books For Young Readers.
- Maini, A. K. (). *Digital electronics : principles, devices and applications*. John Wiley & Sons.
- *Transistors 101*. (n.d.). Adafruit Learning System. <https://learn.adafruit.com/transistors-101/open-collector>
- TTL -Transistor-Transistor Logic Families History and Applications. (2016, April 21). ElProCus - Electronic Projects for Engineering Students. <https://www.elprocus.com/transistor-transistor-logic-ttl/>
- Microcontroller or Processor Multiplexer / Switch. (n.d.). <https://www.ti.com/lit/an/slva704/slva704.pdf>
- Darlington Transistor Pair/Configuration: Working, Application & Examples. (2018). Circuitdigest.com. <https://circuitdigest.com/tutorial/darlington-transistor-pair>
- Proper use of open collector to switch an output. (n.d.). Electrical Engineering Stack Exchange. Retrieved August 17, 2023, from <https://electronics.stackexchange.com/questions/484517/proper-use-of-open-collector-to-switch-an-output>